

# Continuous dynamics

- ▶ **Dynamic system** = system whose state evolves in time
- ► Continuous dynamics = the state is described by continuous functions, its evolution is governed by differential equations
- Example: mechanical, electrical physical processes
  - governed by mechanical / electrical differential equations
  - example:  $m_1 x''(t) + K(x'(t) x_0) = 0$
  - unknown x(t)+ its derivative + second derivative + ...
- Every electrical/mechanical component defines a certain relation between the unknowns

# Electrical systems

#### Electrical systems:

- ► Unknown functions = voltage + current in all branches
- ► Electrical (ideal) elements:
  - resistance:  $u(i) = R \cdot i(t)$
  - ▶ capacitance:  $i(t) = C \cdot \frac{d}{dt}u(t)$
  - etc.
- One big system of linear differential equations (SCS course, basically)
  - ► Kirchhoff equations <=> equations between currents and voltages <=> linear differential equation system
- Example: an RC system (solve at blackboard)

# Mechanical systems

#### Mechanical systems:

- Unknown functions = coordinates x(t), y(t), z(t)
  - speeds = derivatives of the positions
  - acceleration = derivative of speed = second derivative of positions
  - (forces:  $F = m \cdot a = m \cdot \frac{d^2}{dt^2}x(t)$ )
- Mechanical (ideal) elements:
  - ightharpoonup (Consider just a single dimension x(t), is easier)
  - ▶ inertial force:  $F = m \cdot a = m \cdot \frac{d^2}{dt^2} x(t)$
  - friction force:
    - sliding friction:  $\vec{F}_f = -\mu \vec{N} = -\mu \cdot m \cdot \frac{d^2}{dt^2} x(t)$
    - viscous friction:  $\vec{F_v} = -C_v \cdot \vec{v} = -C_v \cdot \frac{d}{dt}x(t)$
  - ▶ etc. . .

# Mechanical systems

- Mechanical elements are described by linear differential equations, just like electrical ones
  - they are just idealizations, physical processes can be highly nonlinear (more complex)
     but wait so are electrical devices actually, and this basn't stopped us
  - but wait, so are electrical devices actually, and this hasn't stopped us. . .
- Example: oscillations after releasing of a loaded spring
  - (solve at blackboard)

# Equivalence spring = LC circuit

▶ A loaded spring oscillates (without any friction) according to the equation:

$$-\frac{1}{m}kx = \frac{d^2x}{dt^2}$$
Spring constant k
$$-\vec{k} = \frac{\vec{k}_{Sp}}{\sqrt{N}}$$
Oscillation

Figure 1: Spring oscillations

▶ image from https://www.youtube.com/watch?v=M2m0ALqgcnQ

# Equivalence spring = LC circuit

► A LC circuit oscillates (without any resistance loss) according to the equation:

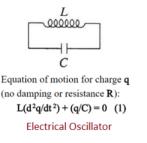


Figure 2: LC oscillations

image from https://www.rfwireless-world.com/Terminology/Mechanical-Oscillator-vs-Electrical-Oscillator.html

# Equivalence spring = LC circuit

- Notice the similarities
- Same linear differential equation:

$$\frac{d^2}{dt^2}f(t) + A \cdot f(t) = 0$$

- ► Same solution
  - ightharpoonup f(t) = sinusoidal (why sinusoidal?)
- ► All kinds of continuous systems can be described in the same way: using linear differential equations

# Electrical - mechanical analogies

- Multiple ways to define analogies between electrical and mechanical characteristics
- ▶ Here is the one we will use from now on:

Electr.	Mech. (linear)	Mech. (rotational)
Current [A]		Torque ("cuplu") [N.m]
voitage [v]	Speed [m/s]	Angular speed [rad/s]

#### Mechanics: linear vs rotational

- ► Note: there are different quantities for **linear** vs **rotational** movements
  - ▶ Force in linear movement ≡ Torque (cuplu) in rotational movement
  - lacktriangle Linear speed linear movement  $\equiv$  Angular speed in rotational movement

# Simple model of a DC motor

- Motor: gateway between the two electrical and mechanical domains
  - converts electric energy to mechanical energy, and vice-versa
- (Simple) model of a DC motor:

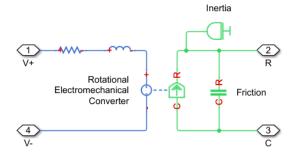


Figure 3: Simple model of a DC motor

Image from Mathworks Simulink (ssc\_dcmotor example model)

### DC motor model: electrical side

#### Electrical side of the DC motor model:

▶ Resistance: models the resistance of the windings

$$u(t) = R \cdot i(t)$$

Inductance: models the inductive behavior of the windings

$$u(t) = L \cdot \frac{d}{dt}i(t)$$

- Controlled voltage source:
  - Voltage ("back electro-magnetic force voltage") is proportional to motor angular speed S(t) on the mechanical side (think of a dynamo)

$$u(t) = K_e \cdot S(t)$$

### DC motor model: mechanical side

#### Mechanical circuit of the DC motor model (no load):

- Controlled force/torque source
  - Generates force/torque proportional to the current i(t) on the electrical side

$$T = K_t \cdot i(t)$$

- ▶ Inertia: models the inertial force of the moving part of the motor
  - Generates force/torque proportional to acceleration (derivative of speed)

$$T_i = -m \cdot acceleration = -m \cdot \frac{d}{dt}S(t)$$

#### DC motor model: mechanical side

#### Mechanical circuit of the DC motor model (no load):

- ► Friction: models the (viscous) friction force of the moving part of the motor
  - Generates force/torque proportional to speed

$$T_f = -C_v \cdot S(t)$$

Inertia and Friction forces/torques oppose the force/torque) of the motor, therefore they have minus sign

# Laplace transform

- ▶ Both electrical and mechanical sides are described by linear differential equations
- ► The Laplace transform is a useful tool (remember SCS)
  - derivation = multiplication by s
  - ightharpoonup integration = multiplication by 1/s
  - ightharpoonup transform function H(s) = output(s)/input(s)
- Exercise: write the equations of all electrical and mechanical elements in Laplace transform

#### Full electrical model

- ▶ All the mechanical elements can be modeled in the electrical domain
  - since they are all just differential equations, basically
  - obtain a full model in the electrical domain only
- Next slides: find electrical correspondent to all mechanical elements

# Model of the controlled voltage source

- ► How to model the controlled voltage source?
- ► Like this:
  - ▶ voltage is proportional to speed:  $U(s) = K_e \cdot S(s)$
  - ▶ speed = integral of acceleration:  $S(s) = S_0 + 1/s \cdot A$
  - ▶ acceleration is proportional to force (force(torque) / mass) =  $C_{const} \cdot T(s)$
  - force/torque = proportional to current:  $T(s) = K_t \cdot I(s)$
- Result:

$$U(s) = K_e \cdot (S_0 + 1/s \cdot C_{const} \cdot K_t I(s))$$

# Model of the controlled voltage source

$$U(s) = \underbrace{K_e \cdot S_0}_{Constant} + \underbrace{K_e C_{const}}_{Constant} \cdot \frac{1}{s} \cdot I(s)$$

- Voltage proportional on integral of current, plus a constant initial value
  - what kind of electrical element acts like this?
- ▶ The controlled voltage source can be modeled as a **capacitance** 
  - Voltage is proportional to integral of current
  - (Current is proportional to derivative of voltage)
  - ► The first constant term = the initial voltage on the capacity
- The equivalent capacitance value depends on the motor parameters

#### Model of the inertial force

- ▶ Inertia = a force which opposes (i.e. reduces) the motor force, and is proportional to acceleration
- ▶ Use the analogy listed before:
  - force = current
  - ► speed = voltage
  - acceleration = derivative of speed = derivative of voltage
- ▶ Inertia = a current which opposes (i.e. reduces) the motor current, and is proportional to derivative of voltage
  - what kind of electrical element acts like this?

#### Model of the inertial force

- ▶ Inertia model = a capacity in parallel with the controlled voltage source
  - ▶ current proportional to derivative voltage ⇔ a capacity
  - ▶ reduces the motor current ⇔ is in parallel with the controlled voltage source (steals some of its current)

#### Model of the friction force

- ► (Viscous) friction = a force which opposes (i.e. reduces) the motor force, and is proportional to speed
- ▶ Use the same analogy:
  - ► force = current
  - speed = voltage
- ► (Viscous) friction = a *current* which opposes (i.e. reduces) the motor *current*, and is proportional to *voltage* 
  - what kind of electrical element acts like this?

#### Model of the friction force

- ► (Viscous) friction model = a **resistance** in **parallel** with the controlled voltage source
  - ► current proportional to voltage ⇔ a resistance
  - ► reduces the motor current ⇔ is in parallel with the controlled voltage source (steals some of its current)

### Model of the sliding friction force

- ► There can also exist a sliding friction force = friction force which does not depend on speed, but is a constant
  - ► that's the friction force you likely encountered in high-school physics ("planul înclinat" etc.)
- Question: how is this force modeled in electrical domain?

# Model of the sliding friction force

- Answer: a constant current source in parallel
  - ▶ constant current ⇔ constant source
  - ▶ in parallel ⇔ reduces the motor current

#### The full electrical model

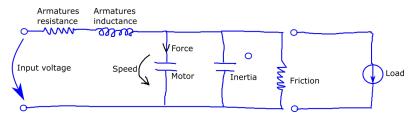


Figure 4: DC Motor electrical equivalent model

- ► This is a second order model (1L, 1C)
  - the two capacities are in parallel, so they can be added into a single one
- ▶ The L is the inductance of the armatures ⇒ small, often negligible
- Can be approximated by a first order model

### Transfer function of a DC motor

- We can derive a transfer function
  - ightharpoonup input = voltage on motor input U(s)
  - output = motor speed S(s) = voltage on equivalent motor capacity
- ▶ Transfer function  $(2^n d \text{ degree, approximately } 1^{st} \text{ degree})$

$$H(s) = \frac{S(s)}{U(s)} = \frac{b_0 s + b_1}{s^2 + a_1 s + a_2} \approx \frac{K}{\tau \cdot s + 1}$$

- Take home message:
  - Simple DC motor no-load model = a second order RLC model = approx a RC model
  - Behaves like a RC low-pass filter
- ▶ Note: This is a no-load model (motor doesn't move anything heavy)

#### Motor under load

- What happens if motor has a load?
  - e.g. the motor drags/lifts a constant weight
  - i.e. like a crane lifting a big weight from the ground
- ► How to model the load?

#### Motor under load

- ► How to model the load?
- ► Like a constant force/torque opposing the motor force/torque
  - ▶ i.e. like a sliding friction force
  - i.e. like a current source in parallel, stealing lots of current
- ▶ In practice, the load force/torque may not be constant
  - depends on mechanical properties
  - e.g. lifting the hatch/liftgate ("portbagaj") of a car: harder when lower, easier when higher

### Simulink model

- ► Simulink has a DC motor model already integrated
- ➤ You will use it in the lab (maybe)

#### What to use the model for?

What to use the motor model for?

#### Simulate:

- how fast motor starts when supply is first applied
- what happens when supply fluctuates (e.g. PWM)
- what happens when motor parameters change (e.g. temperature rises, friction slows)
- what happens when load varies
- **...**

### Motor speed controller

Basic problem: how to make sure motor speed stays **exactly** as desired:

- even if parameters vary
- even if load varies
- even if supply varies
- on power on, speed is reached as fast as possible

This is a job for a motor controller

► Today's special: the PID motor controller

#### Motor controllers

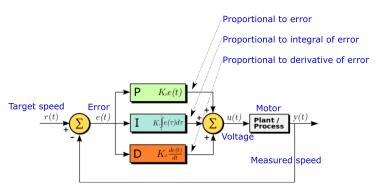


Figure 5: PID speed controller (image from Wikipedia)

- Negative feedback loop
- Can be used for any sort of process, not just motors
- Make output signal y(t) follow the desired input r(t)

#### PID Controller

- ▶ PID controller = the simplest solution
- ▶ Input = error signal = target speed actual measured speed
- Output = Sum of three components:
  - ▶ Proportional: *P* \* input
  - ► Integral: / \* integral of input
  - ▶ **D**erivative: *D* \* derivative of input

### PID Controller - P component

- ▶ Intuitive role of the *P* component:
  - ▶ If actual speed < target => increase motor voltage
  - ► If actual speed > target => decrease motor voltage
- ► This is not enough:
  - Non-zero motor voltage requires non-zero speed error => the motor never actually reaches the target speed
  - ► There is always a small systematic error ("bias error", "steady-state error")

# PID controller - only P, systematic error



Figure 6: Systematic error for P-only controller

### PID Controller - I component

- ▶ Intuitive role of the *I* component:
  - ▶ Eliminate the bias error of the *P* component, by slowly integrating the remaining error signal => integral slowly increases over time => motor voltage is pushed towards the correct value
  - ► Error signal cannot remain constant forever, because the integral would grow large => force changes to the motor input

### PID controller - P and I

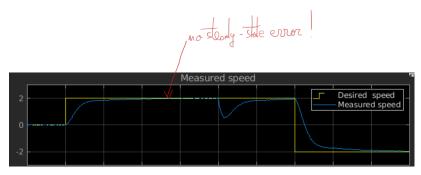


Figure 7: P and I components

### PID Controller - D component

- ▶ Intuitive role of the *D* component:
  - make the system react faster (jumpy) to fast input changes
  - improves system reaction time
- ▶ Problem:
  - fast reaction time = more oscillation behavior:
    - more overshoot
    - possibly unstable

### PID controller - P, I and D

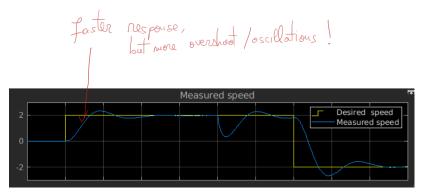


Figure 8: P, I and D components

# PID tuning

- PID tuning: find P, I, D values for good behavior
  - Typical requirements:
    - stable system, overall
    - overshoot not larger than X%
    - fastest response in these conditions
- Find out more at the Vehicle Control Systems course (2nd semester, I think)